

# Sensors, Measurements & Instrumentation

Papa Kofi Boahen

October 14, 2022

Roll Number: 10211100334

BSc Computer Engineering

## Question 1

Resistance of galvanometer,  $R_G = 5\ \Omega$

Current through galvanometer,  $I_G = 15 \times 10^{-3}\ \text{A}$

Current through shunt resistor,  $I_{R_{sh}}$


Voltage across galvanometer,  $V_G$

Voltage across shunt resistor,  $V_{sh}$

Voltage across multiplier resistor,  $V_M$

Resistance of shunt,  $R_{sh}$


Resistance of multiplier,  $R_M$

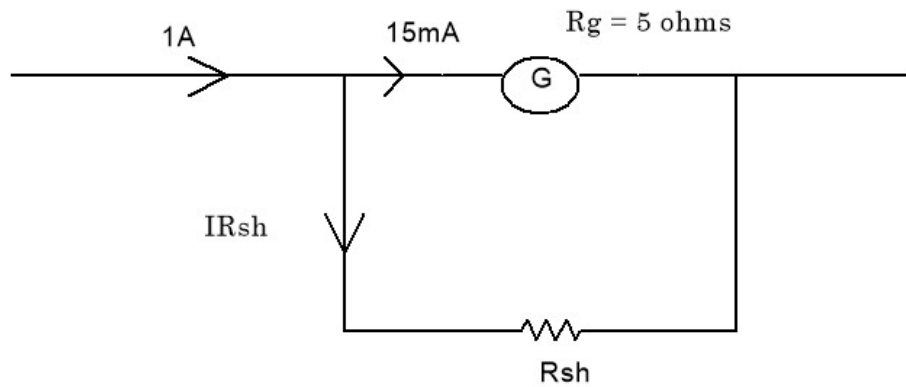

$$I) \quad I_{R_{sh}} = 1 - (15 \times 10^{-3})$$
$$I_{R_{sh}} = 0.985 \text{ A}$$

$$\begin{aligned}
 V_G &= V_{sh} \\
 I_G R_G &= I_{R_{sh}} R_{sh} \\
 R_{sh} &= \frac{I_G R_G}{I_{R_{sh}}} \\
 &= \frac{15 \times 10^{-3} \times 5}{0.985} \\
 &= \underline{\underline{0.076 \Omega}}
 \end{aligned}$$

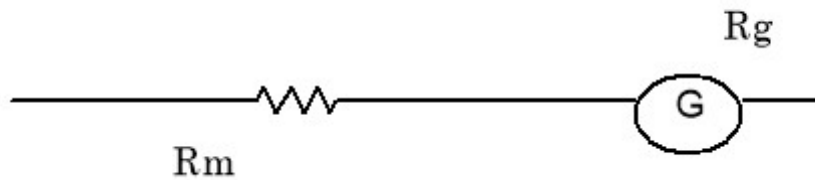Total voltage through multiplier and galvanometer,  $V$



$$II) \quad V = V_M + V_G$$


$$V = I_G R_M + I_G R_G$$

$$R_M = \frac{V - I_G R_G}{I_G}$$

$$R_M = \frac{15 - (15 \times 10^{-3}) \times (5)}{(15 \times 10^{-3})}$$

$$R_M = \underline{\underline{995 \, \Omega}}$$

## Question 2

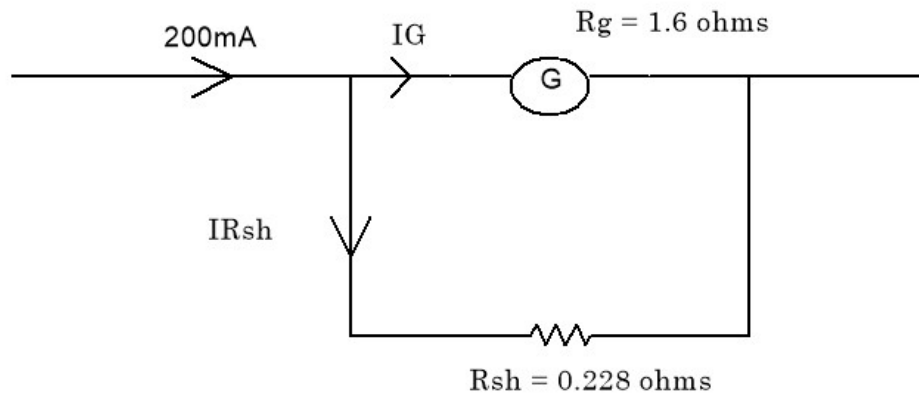

$$V_G = V_{R_{sh}} \quad I_{R_{sh}} = 0.2 - I_G$$


$$I_G R_G = I_{R_{sh}} R_{sh}$$

$$I_G R_G = 0.2 R_{sh} - I_G R_{sh}$$

$$I_G R_G + I_G R_{sh} = 0.2 R_{sh}$$


$$\begin{aligned} I_G &= \frac{0.2 R_{sh}}{R_G + R_{sh}} \\ &= \frac{0.2 \times 0.228}{1.6 + 0.228} \\ &= 0.0249 \\ &= \underline{\underline{24.9 \text{ mA}}} \end{aligned}$$

### Question 3

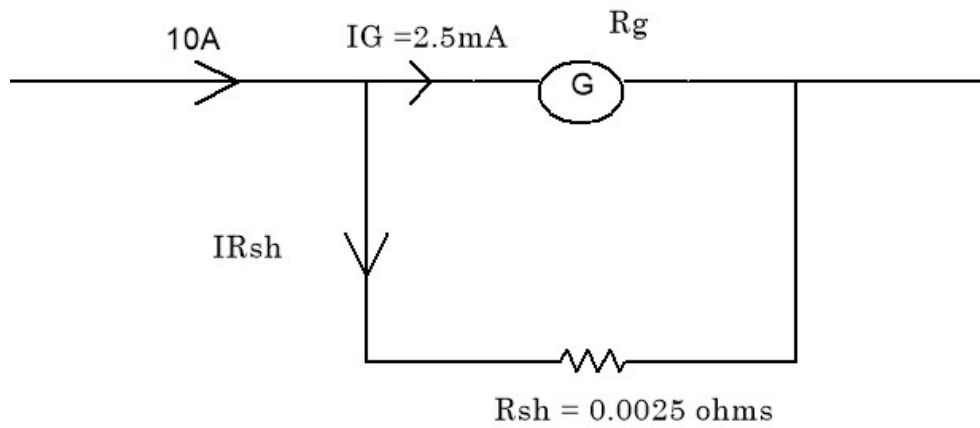

$$\begin{aligned}
 I_{R_{sh}} &= 10 - (2.5 \times 10^{-3}) \\
 I_G R_G &= I_{R_{sh}} R_{sh} \\
 R_G &= \frac{9.9975 \times 0.0025}{2.5 \times 10^{-3}} \\
 &= \underline{\underline{9.9975 \Omega}}
 \end{aligned}$$

### Question 4

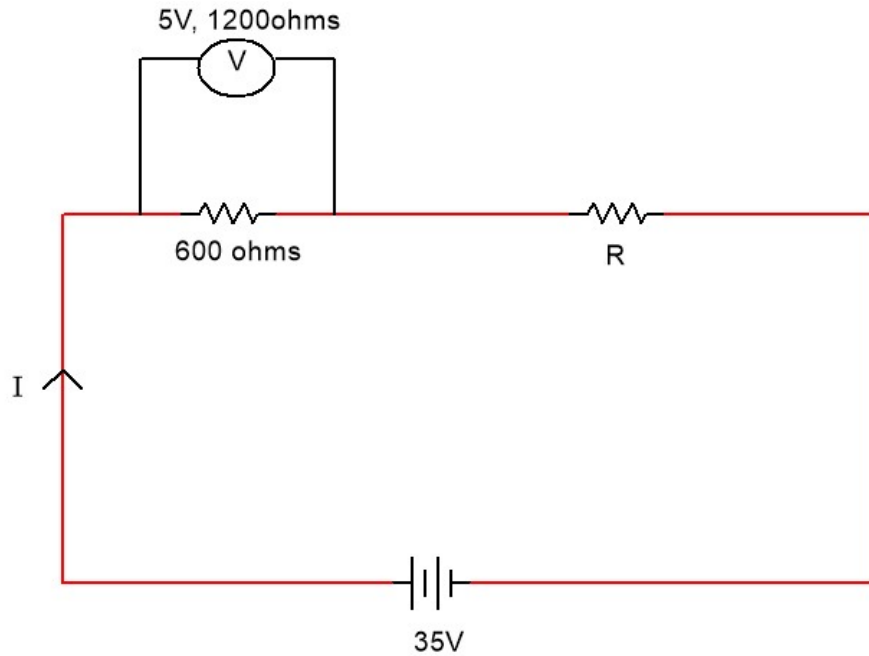

Resistance across parallel connection

$$\begin{aligned} R_{\parallel} &= \frac{1200 \times 600}{1200 + 600} \\ &= 400\Omega \end{aligned}$$

$$\begin{aligned}
 V &= IR_{\parallel} \\
 I &= \frac{V}{R_{\parallel}} \\
 &= \frac{5}{400} \\
 &= \frac{1}{80} \text{ A}
 \end{aligned}$$

*Voltage across R :  $35 - 5 = 30 \text{ V}$*

$$\begin{aligned}
 R &= \frac{V}{I} = \frac{30}{1/80} \\
 &= \underline{\underline{2400\Omega}}
 \end{aligned}$$